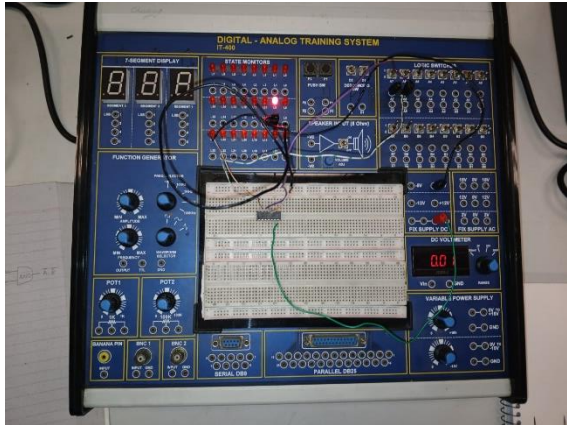



LAB 5 PHOTOGRAPHS

DE MORGAN'S 1st THEORM:



NAND Gate

=

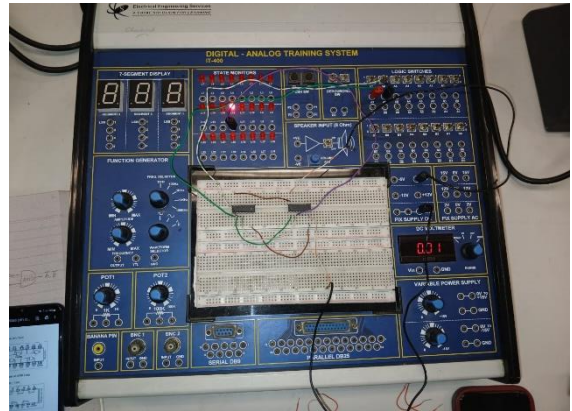


OR Gate with Inverted

DE MORGAN'S 2nd THEORM:



NOR Gate

=

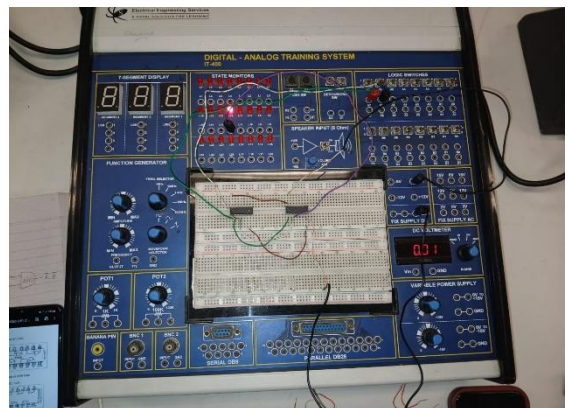

AND Gate with Inverted inputs